



RESEARCH DEPARTMENT

A TELEVISION CHECK RECEIVER FOR BAND I, CHANNEL 1

Report No. G-064

(1955/55)

**THE BRITISH BROADCASTING CORPORATION
ENGINEERING DIVISION**

RESEARCH DEPARTMENT

A TELEVISION CHECK RECEIVER FOR BAND I, CHANNEL 1

Report No. G-064

(1955/35)

R.E. Jones

C. G. Mayo, M.A., B.Sc., M.I.E.E.

W. Proctor Wilson

(W. Proctor Wilson)

This Report is the property of the British Broadcasting Corporation and may not be reproduced or disclosed to a third party in any form without the written permission of the Corporation.

A TELEVISION CHECK RECEIVER FOR BAND I CHANNEL 1

Section	Title	Page
	SUMMARY	1
1	INTRODUCTION	1
2	DESCRIPTION OF RECEIVER	1
	2.1. General	1
	2.2. Aerial Amplifier	3
	2.3. Transmission Line	4
	2.4. Input Attenuator	4
	2.5. Filter Pre-amplifier	4
	2.6. Sound-Carrier Rejection Filter	4
	2.7. Main Amplifier and Demodulator	7
3	PERFORMANCE	7
4	OPERATING INSTRUCTIONS	9
5	CONCLUSIONS	11
6	REFERENCES	11

November 1955

Report No. G-064

(1955/35)

A TELEVISION CHECK RECEIVER FOR BAND I, CHANNEL 1

SUMMARY

A television receiver suitable for picture-quality checking is described; it is designed for the reception of double-sideband signals on Channel 1, vision carrier 45 Mc/s. The receiver gives negligible phase and amplitude distortion of modulation frequencies up to 3 Mc/s, and provides 35 dB suppression of the sound carrier on 41.5 Mc/s. The output contains full synchronising pulses and the d.c. component; the peak-white signal level across an external load of 75 ohms is 1 volt.

1. INTRODUCTION

The receiver to be described was designed for checking the quality of television pictures at Kingswood Warren from the Alexandra Palace transmitter; the path length is approximately 21 miles (34 km). Alexandra Palace radiates double-sideband transmissions, and the field strength at 30 ft (9.1 m) above ground level is approximately 4 mV/m. The field strength of stations operating in adjacent channels is low, so that the selectivity of the receiver is not very important. There is, however, the possibility of interference due to locally generated noise. Since the equipment may be used for observing the effect of noise on television pictures it was desirable to minimise the pick-up of local interference.

An inverted-V receiving aerial¹, located in the grounds at Kingswood Warren, is used; it is approximately 300 yards (270 m) from the television laboratories. The aerial is connected to an amplifier and thence by a balanced line to the main receiver in the television laboratories. After passing through an attenuator and amplifier, the signal passes through the sound-carrier filter and thence through another amplifier to the demodulator. The output of the demodulator is intended to be fed to a high-quality commercial monitor. Fig. 1 shows a block schematic of the complete system, together with the approximate operating levels.

2. DESCRIPTION OF RECEIVER.

2.1. General.

The basic design of the amplifiers is simple and conservative. As suppression of interfering signals in adjacent channels is not important*, no attempt was made to use the valve and incidental stray capacities as elements in stop filters. It was considered that, in the unlikely event of interference from other stations,

* in view of the purpose for which the receiver was designed.

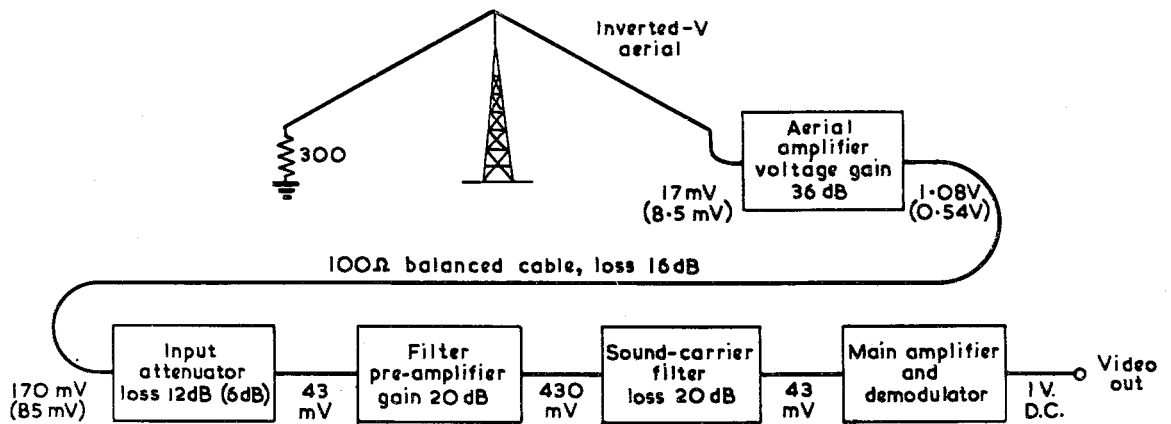


Fig. 1 - Block schematic of complete system

The levels given are the peak white, r.m.s. values of the Alexandra Palace vision carrier.
The levels in brackets apply when the reserve transmitter is in use.

this could be dealt with by additional stop filters. The general principle adopted, therefore, is to use amplifying stages in which the stray capacitances are tuned with parallel inductances, each circuit being loaded with a suitable parallel resistance.

For one such circuit the variation of the stage gain with frequency may be written:

$$\frac{V_{r+1}}{V_r} = \frac{\mu_0}{(1+\lambda p)} \quad (1)$$

where V_r and V_{r+1} are the voltages across the anode circuits in the r th and $(r+1)$ th stages respectively

μ_0 is a constant

$p = ix$ where x is the frequency deviation from the carrier, normalised such that $x = \pm 1$ at a deviation of $\pm 3\text{Mc/s}$

λ is a factor proportional to the loading resistance (λ is assumed to be $\ll 1$).

The modulus of expression (1) may be written

$$\left| \frac{V_{r+1}}{V_r} \right| = \frac{\mu_0}{\sqrt{1+\lambda^2 x^2}} \approx \mu_0 \left(1 - \frac{\lambda^2 x^2}{2} \right) \quad (2)$$

If ϕ is the phase difference between V_r and V_{r+1} , the normalised group delay, $\left. \begin{array}{l} \text{with} \\ \lambda x \ll 1 \end{array} \right\}$

$$\frac{d\phi}{dx} = - \frac{\lambda}{(1+\lambda^2 x^2)} \approx -\lambda (1-\lambda^2 x^2) \quad (3)$$

and the time delay is $\frac{\lambda}{6\pi} (1-\lambda^2 x^2) \mu\text{s}$. The first term is the group delay, and the second term is the group-delay distortion.

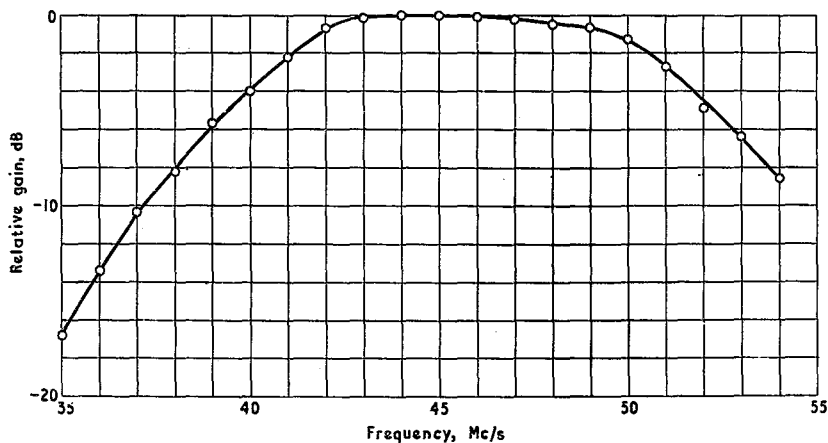


Fig. 3 - Frequency response of aerial amplifier

2.3. Transmission Line.

The transmission line used for coupling the aerial amplifier to the main amplifier in the television laboratories is balanced, and has a solid polythene dielectric. The characteristic impedance is 100 ohms; the attenuation is approximately 16 dB.

2.4. Input Attenuator.

The transmission line is terminated in a 100-ohm balanced to 100-ohm unbalanced transformer, which feeds a 6-step attenuator, each step being 3 dB. This enables the output voltage of the receiver to be adjusted to the correct value, i.e. to give the required video output of approximately 1 volt peak white.

2.5. Filter Pre-amplifier.

This is similar in design to the aerial amplifier. The circuit diagram is shown in Fig. 4; the gain at the mid-band frequency is 20 dB, and the output is a balanced circuit of 100 ohms impedance.

2.6. Sound-carrier Rejection Filter.

The filter was required to provide adequate suppression at 41.5 Mc/s and to pass frequencies exceeding 42 Mc/s with minimum phase distortion. To secure the high discrimination required, two alternative methods presented themselves. One was by means of subtractive methods such as bridges balanced at the frequency to be rejected, of which the bridged-T circuit is an example. It is difficult, using this method, to secure adequate rejection bandwidth without incurring serious phase distortion elsewhere in the band, unless high Q coils are used. On the other hand, if high Q coils are available, subtractive methods are unnecessary; a conventional confluent band-stop filter becomes the more practical proposition.

It was found that Q's of the order of 600 could be obtained with coils of about 12 turns of 0.08 in. (2 mm) diameter tinned copper wire on 1.12 in. (2.8 cm) diameter porcelain formers with air-spaced trimming condensers. Larger inductances

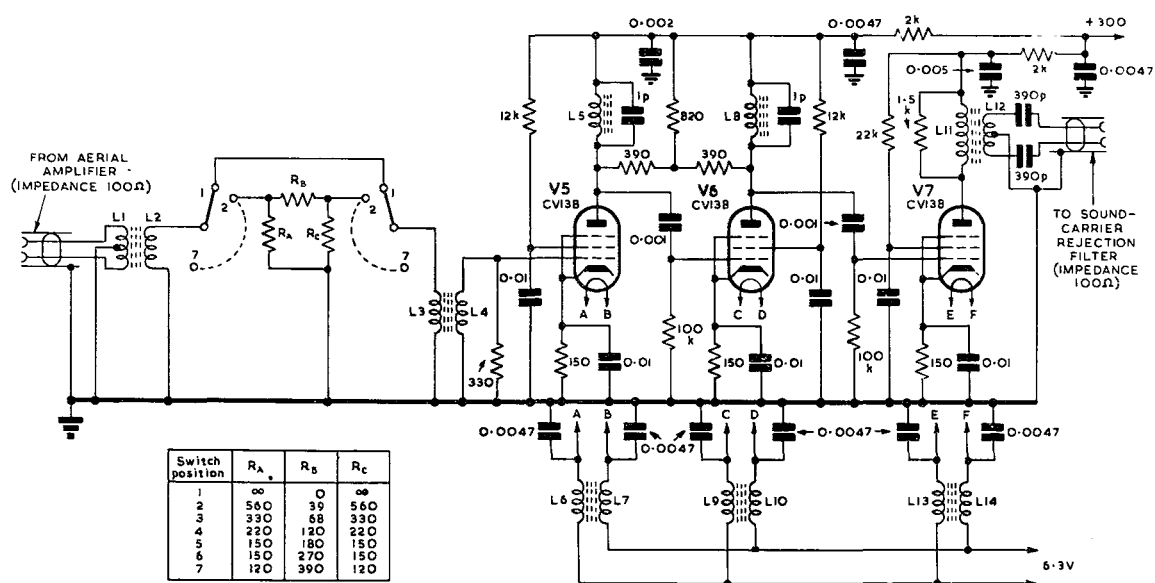


Fig. 4 - Circuit diagram of input attenuator and filter pre-amplifier

were unusable owing to the effect of stray capacitances, while smaller inductances necessitated larger capacitances which in practice have greater losses. There is therefore an optimum working impedance for the actual tuned circuits, and the filter was designed to use such coils, other artifices being used to "fit" the tuned circuits into the filter structure.

The relatively small spacing between the stop and pass frequencies necessitates a high impedance ratio between the series and shunt elements of the confluent band-stop filter. The low impedance series element was therefore made a single turn loop of 0.064 in. (1.6 mm) diameter copper wire, 0.38 in. (0.95 cm) diameter, coupled to a parallel tuned circuit of the type described above. The coupling was made variable in order to adjust the ratio of the transformer thus formed, the setting being a compromise to give the greatest rejection at 41.5 Mc/s with tolerable amplitude distortion at 42 Mc/s. The inductance of the single turn, 0.03 μ H, is virtually the series leakage inductance of this otherwise ideal transformer. At frequencies other than the stop frequency, the series reactance will be approximately j8 ohms compared with the characteristic impedance of the filter which is 4 ohms. It is therefore necessary to tune out the reactance of this coil by means of a series condenser which gives a final series impedance over the band of about 1 ohm. This can be neglected relative to the shunt admittance present at the pass frequencies.

The shunt element consists of a series-tuned coil similar to the series coil but connected without impedance transformation. At 41.5 Mc/s both the series and the shunt elements are resonant, the series circuit to maximum impedance and the shunt circuit to minimum impedance, thus giving an attenuation nearly equal to the ratio of their impedances. At higher frequencies the series element looks like a capacitance whereas the shunt element looks like an inductance. This gives a peak in the response curve at 41.7 Mc/s which, with a normally loaded filter, would be almost exactly smoothed out, but at the expense of phase distortion. By increasing the coupling of the series element, the attenuation at 41.5 Mc/s can be increased, at the

same time increasing the magnitude of the peak at 41.7 Mc/s. A compromise was made which gave an attenuation of 34 dB at 41.5 Mc/s and a peak of +4 dB at 41.7 Mc/s. There is a rise of about 1 dB at 42 Mc/s which is compensated by the overall selectivity of the receiver.

As the Q of the filter is high, it is necessary to use capacitive potential dividers to provide a sufficiently smooth adjustment of the resonant frequency of the tuned circuits. This is provided by a miniature pre-set condenser employing P.T.F.E. insulation with a 22 pF silvered mica condenser. While mica insulation has too great a loss to be used in the main tuning condenser, it is quite satisfactory for use in a potential divider with a step down of approximately 10:1. The final trimmer is a 2-8 pF concentric type which is accessible through a hole in the coil screen.

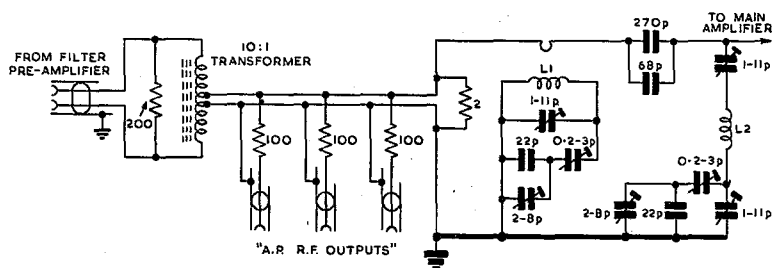


Fig. 5 - Circuit diagram of sound-carrier rejection filter

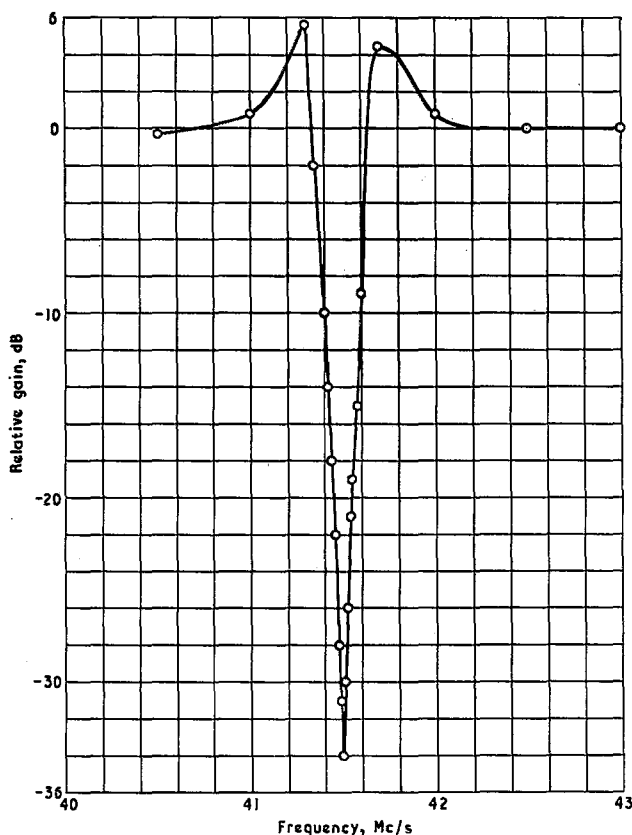


Fig. 6 - Sound carrier rejection filter response

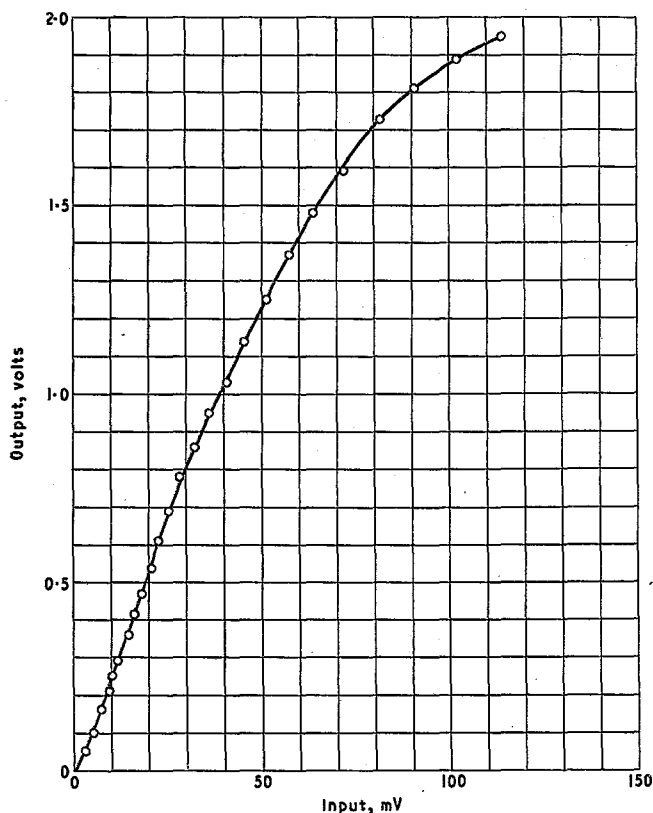


Fig. 8 - Input-output characteristic of main receiver
(measured at 45 Mc/s, input attenuator 0 dB)

measured under the same conditions. Summarising these results, the overall frequency response is within $\pm \frac{1}{2}$ dB over the vision passband of 45 ± 3 Mc/s. The sound-carrier is suppressed 35 dB relative to the vision carrier, and this amount of rejection has proved satisfactory in practice. The modulation frequency response is flat to within $\pm \frac{1}{2}$ dB for all frequencies up to 3.2 Mc/s; the group delay is constant at $0.22 \mu\text{s}$ for frequencies up to 2.7 Mc/s and rises by $0.06 \mu\text{s}$ at 3 Mc/s.

The effect of temperature on the sound carrier rejection filter has been measured; the frequency of maximum rejection decreases with an increase in temperature by approximately 1 kc/s per degree centigrade, while the amount of attenuation remains constant. Thus a rise of temperature of 10°C will reduce the attenuation at 41.5 Mc/s by 4 dB if the filter is not retrimmed.

The aerial amplifier has a linear input-output characteristic for inputs up to 27 mV r.m.s.; the corresponding output level is 1.7 V r.m.s. If the input rises above the former value an attenuator having an impedance of 300 ohms should precede the aerial amplifier, otherwise there may be intermodulation between the sound and vision carriers.

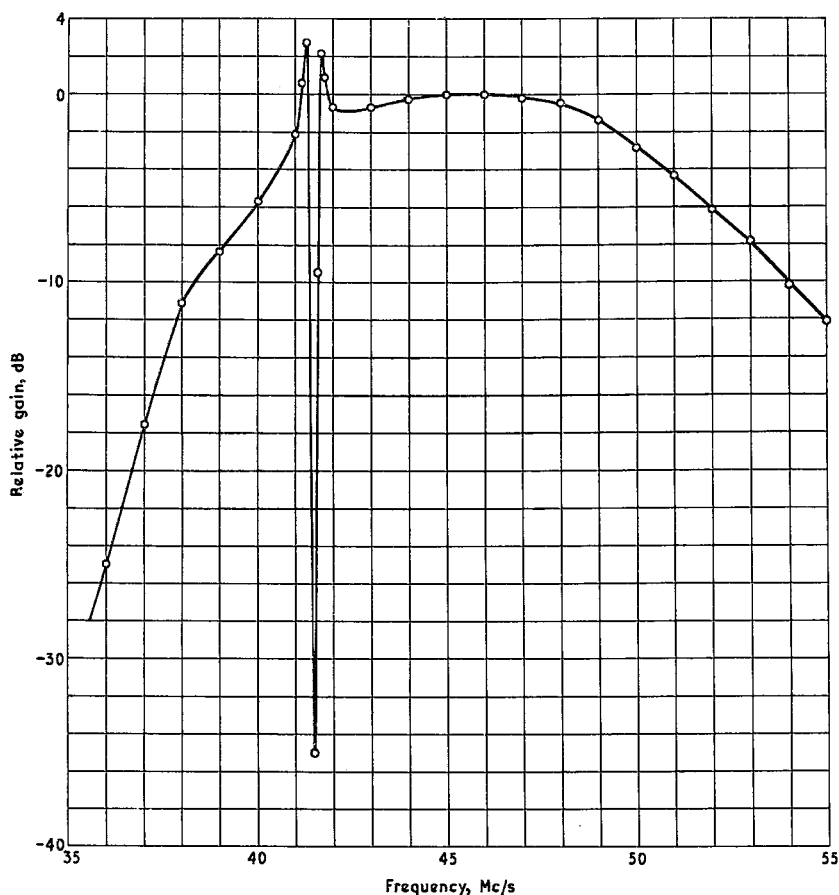


Fig. 9 - Overall frequency response (omitting transmission line)

4. OPERATING INSTRUCTIONS.

The input attenuator should be set to give a peak output of 1 volt across 75 ohms. This can be achieved with a range of signal levels of 40-320 mV at the input of the main receiver. In addition to the demodulated output a double-sideband television signal with sound carrier is available at the sockets marked A.P.R.F. outputs; the open-circuit voltage at these points is approximately 40 mV. The outputs may be loaded or even short-circuited without affecting the performance of the receiver.

The operating anode current of each CV138 valve in the receiver is nominally 10 mA with a screen current of approximately 2.5 mA. The two Z309 valves used should each take an anode current of 20 mA and a screen current of approximately 5.3 mA. The total H.T. current of the aerial amplifier is therefore 50 mA. The main receiver takes 126 mA, of which 38 mA is taken by the filter pre-amplifier and 88 mA by the main amplifier.

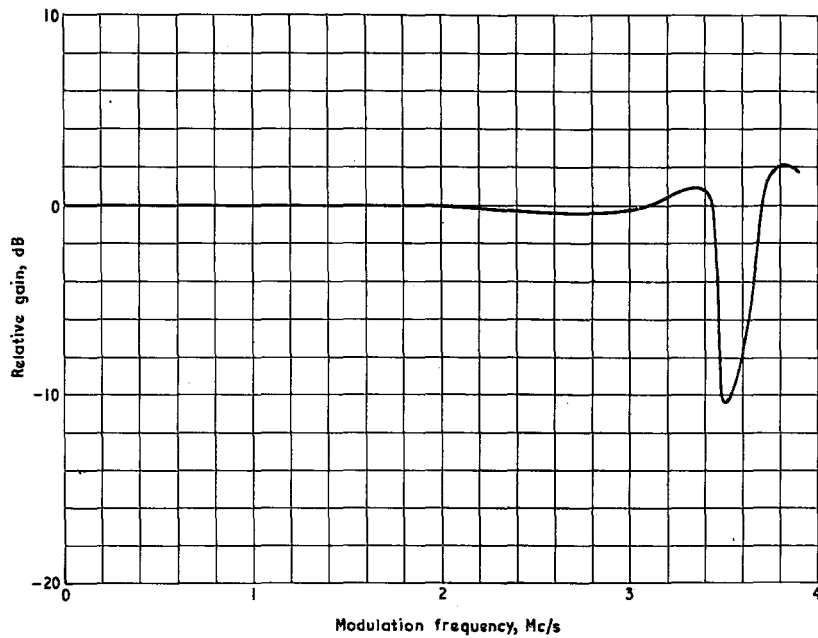


Fig. 10 - Modulation-frequency response

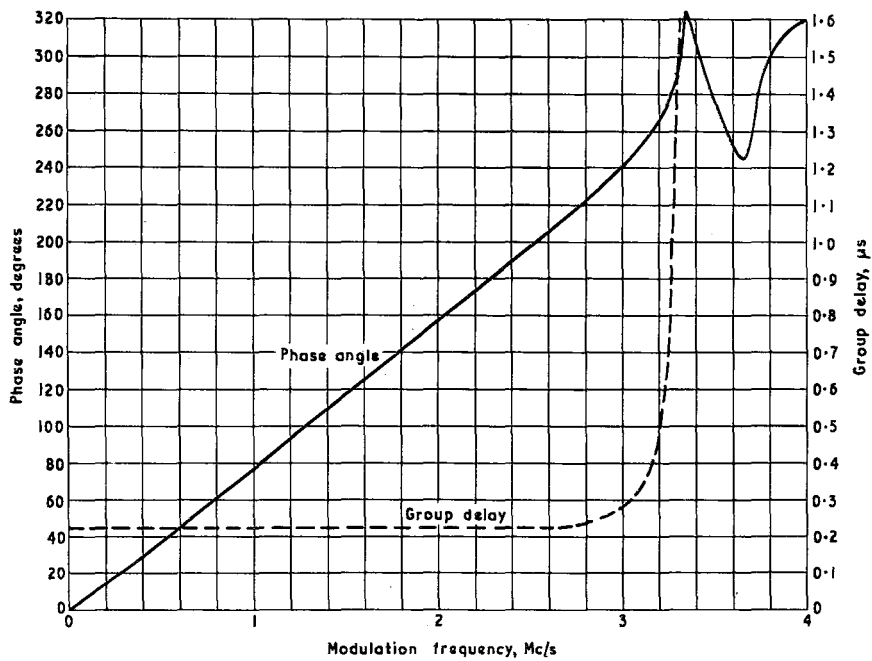


Fig. 11 - Overall phase response and group delay

5. CONCLUSIONS .

A television receiver has been produced which is capable of providing a television waveform virtually free from amplitude and phase distortion, with adequate rejection of the associated sound channel.

6. REFERENCES .

1. "Vertical Half-Rhombic Aerial for Television on 45 Mc/s", Research Department Technical Memorandum No.G1005, April, 1950.